MAT 107: Exam 1 Winter — 2022 01/08/2023 Time Limit: ' ∞ '

Name:	Caleb M ^c Whorter — Solutions	

Write your name on the appropriate line on the exam cover sheet. This exam contains 11 pages (including this cover page) and 10 questions. Check that you have every page of the exam. Answer the questions in the spaces provided on the question sheets. Be sure to answer every part of each question and show all your work. If you run out of room for an answer, continue on the back of the page — being sure to indicate the problem number.

Question	Points	Score
1	10	
2	10	
3	10	
4	10	
5	10	
6	10	
7	10	
8	10	
9	10	
10	10	
Total:	100	

MAT 107: Exam 1 2 of 11

1. (10 points) Construct the logic table for $P \to (\neg P \lor Q)$.

Solution.

P	Q	$\neg P$	$\mid \neg P \lor Q \mid$	$P \to (\neg P \lor Q)$
\overline{T}	T	F	T	T
T	F	F	F	F
F	T	T	T	T
F	F	T	T	T

MAT 107: Exam 1 3 of 11

2. (10 points) Show that $\neg(P \to Q)$ and $P \land \neg Q$ are logically equivalent.

Solution.


$P \mid Q$	$ P \rightarrow Q$	$\mid \neg(P \to Q) \mid$	$\neg Q$	$P \wedge \neg Q$
$T \mid T$	\parallel T	\mathbf{F}	F	\mathbf{F}
$T \mid F$	\parallel F	\mathbf{T}	T	${f T}$
$F \mid T$	\parallel T	\mathbf{F}	F	${f F}$
$F \mid F$	$\parallel T$	\mathbf{F}	T	${f F}$

Because the bolded columns have the same logical outputs for the same logical inputs, we know that $\neg(P \to Q)$ and $P \land \neg Q$ are logically equivalent; that is, $\neg(P \to Q) \equiv P \land \neg Q$. Alternatively, using the fact that $P \to Q \equiv \neg P \lor Q$, we have...


$$\neg(P \to Q) \equiv \neg(\neg P \lor Q) \equiv \neg(\neg P) \land \neg Q \equiv P \land \neg Q$$

MAT 107: Exam 1 4 of 11

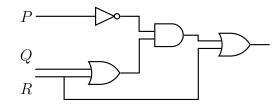3. (10 points) Find the logical expression corresponding to the following circuit:



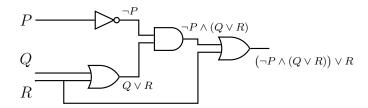Solution. We follow each wire, labeling the outputs of each circuit.



Therefore, the logical expression corresponding to the given circuit is...

$$(\neg P \land (Q \lor R)) \lor R$$

MAT 107: Exam 1 5 of 11

4. (10 points) Find a logical expression corresponding to a circuit whose on/off table is given below:

P	Q	R	?
1	1	1	1
1	1	0	0
1	0	1	0
1	0	0	0
0	1	1	0
0	1	0	1
0	0	1	0
0	0	0	1

Solution. We look each row and ' \land ' each input (possibly negating the input so that it is 1):

P	Q	R	?		
1	1	1	1		$P \wedge Q \wedge R$
1	1	0	0		
1	0	1	0		
1	0	0	0		
0	1	1	0		
0	1	0	1	\leftarrow	$\neg P \land Q \land \neg R$
0	0	1	0		
0	0	0	1	\leftarrow	$\neg P \wedge \neg Q \wedge \neg R$

We then ' \lor ' these expressions together to create a logical expression corresponding to the circuit whose on/off table given:

$$(P \land Q \land R) \lor (\neg P \land Q \land \neg R) \lor (\neg P \land \neg Q \land \neg R)$$

MAT 107: Exam 1 6 of 11

5. (10 points) Convert the following to base-10:

- (a) 1110011₂
- **(b)** 4501₆
- (c) cal_{16}

Solution.

(a)

$$1110011_{2}$$

$$1 \cdot 2^{0} + 1 \cdot 2^{1} + 0 \cdot 2^{2} + 0 \cdot 2^{3} + 1 \cdot 2^{4} + 1 \cdot 2^{5} + 1 \cdot 2^{6}$$

$$1 + 2 + 0 + 0 + 16 + 32 + 64$$

$$115$$

(b)

$$4501_{6}$$

$$1 \cdot 6^{0} + 0 \cdot 6^{1} + 5 \cdot 6^{2} + 4 \cdot 6^{3}$$

$$1 + 0 + 180 + 864$$

$$1045$$

(c)

$$\begin{aligned} \text{ca1}_{16} \\ 1 \cdot 16^0 + \text{a} \cdot 16^1 + \text{c} \cdot 16^2 \\ 1 \cdot 16^0 + 10 \cdot 16^1 + 12 \cdot 16^2 \\ 1 + 160 + 3072 \\ 3233 \end{aligned}$$

6. (10 points) Convert the following base-10 numbers to the indicated base-*b* numbers:

(a)
$$27, b = 2$$

(b)
$$654, b = 7$$

(c)
$$1492$$
, $b = 16$

Solution.

(a)

27	
13	1
6	1
3	0
1	1
0	1

$$27 = 11011_2$$

(b)

654	
93	3
13	2
1	6
0	1

$$654 = 1623_7$$

(c)

$$1492 = 5 \mathrm{d} 4_{16}$$

MAT 107: Exam 1 8 of 11


7. (10 points) Consider a subtraction game with perfect players and subtraction $S = \{1, 3, 5\}$. Show you go first or second if there are 2023 coins? If you should go first, what is a winning move?

Solution. It is clear that 0 is a P position (the *previous* player took the last chip and won). If there is one chip left, the *next* player can take the final chip and win. Therefore, 1 is an N-position. If there are two chips left, the only possible move is to take a single chip to a P-position. Therefore, two chips are a P-position. Continuing this way, labeling the positions whose only valid moves are to previously labeled N-positions as P-positions and positions that have a valid move to a P-position as an N-position, we obtain the following chain of P, N-positions:


The pattern of PN repeats. Observe that each even position is a P-position and each odd position is an N-position. Because 2023 is odd, it must be an N-position. You need to make a move to change the number of coins to an even number. Taking away either one, three, or five coins will result in an even number of coins remaining.

MAT 107: Exam 1 9 of 11

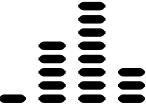8. (10 points) Explain why you should go first in the game of NIM below. What is a winning opening move?



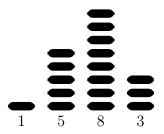Solution. First, we count the number of coins in each pile:



We then write each of these numbers in binary. We $1 = 1_2$, $5 = 101_2$, $8 = 1000_2$, and $3 = 11_2$. We can then add these numbers in binary without carrying (adding preceding 0's for ease of reading:

Because the NIM-sum is $1111 \neq 0000$, this must be an N-position. Therefore, the *next* player to move has a winning move. Therefore, you want to go next, i.e. first. A winning move is a move which results in a NIM-sum of zero. Clearly, the 1 in the far left needs to be changed to a zero, which can only happen by removing chips from the 8-pile. We need a 1 in the remaining three columns to result in a NUM-sum of 0 in these columns. But then we need change the 8-pile from $8 = 1000_2$ to $0111_2 = 7$. Therefore, the only winning move is to remove a single chip from the 8-chip pile.

MAT 107: Exam 1 10 of 11

9. (10 points) Nancy and Drew are taking out a simple discount note to pay for a cruise. This loan will be for \$3,800 for 3 months at 9.6% yearly interest. How much do they receive from the bank?

Solution. In a simple discount note, the discount (interest) is paid up-front. One then receives the maturity (loan amount) minus this discount (interest). So the amount received (the proceeds) is given by...

$$P = M - D$$

where M is the maturity and D is the discount. We know that D=Mrt, where r is the annual interest rate and t is the time (in years). But then...

$$D = Mrt = \$3,800 \cdot 0.096 \cdot \frac{3}{12} = \$91.20$$

Then we have...

$$P = M - D = \$3,800 - \$91.20 = \$3,708.80$$

Therefore, Nancy and Drew receive \$3,708.80 from the bank.

MAT 107: Exam 1 11 of 11

10. (10 points) Suppose that you invest \$7,000 into an account which earns 2.3% annual interest, compounded quarterly. Will you have \$10,000 in the account after 6 years? Explain. If not, how long until the account contains \$10,000?

Solution. The future value, F, of a principal amount, P, earning r annual interest, compounded k times per year for t years is given by...

$$F = P\left(1 + \frac{r}{k}\right)^{kt}$$

The principal amount is P = \$7,000. We know that r = 0.023 and because the interest is compounded quarterly, i.e. four times per year, k = 4. But then after t = 6 years, this investment will be worth...

$$F = P \left(1 + \frac{r}{k} \right)^{kt}$$

$$= \$7000 \left(1 + \frac{0.023}{4} \right)^{4.6}$$

$$= \$7000(1.00575)^{24}$$

$$= \$7000(1.14752192)$$

$$= \$8,032.65$$

Therefore, after 6 years, the investment will only be worth \$8,032.65—not the desired \$10,000. We know the time for an investment to raise from a principal P to a future value F is given by $t = \frac{\log(F/P)}{k \log(1+r/k)}$. But then...

$$t = \frac{\log(F/P)}{k \log(1 + r/k)}$$

$$= \frac{\log(10000/7000)}{4 \log(1 + \frac{0.023}{4})}$$

$$= \frac{\log(1.42857143)}{4 \log(1.00575)}$$

$$= \frac{0.35667494}{0.02293413}$$

$$= 15.55 \text{ years}$$

Therefore, it will take 15.55 years for the \$7,000 investment to be worth \$10,000.